

# Programmable Processors

Control Unit

- Instruction memory (ROM): 128 X 16
- Data memory (RAM): 256 X 16
- Register file: 16 X 16
- ALU: Two 16-bit inputs, 16-bit output

**Refresh – The Sizes of Things**

- Instruction Set – List of allowable instructions and their representation in memory
- Each of our instructions is **16 bits** long
- Most of them contain some address information
- General form : **operation source destination**

**NOOP** instruction – **0000 0000 0000 0000**

**STORE** instruction – **0001**  $r_3r_2r_1r_0$   $d_7d_6d_5d_4d_3d_2d_1d_0$

**LOAD** instruction – **0010**  $d_7d_6d_5d_4d_3d_2d_1d_0$   $r_3r_2r_1r_0$

**ADD** instruction – **0011**  $ra_3ra_2ra_1ra_0$   $rb_3rb_2rb_1rb_0$   $rc_3rc_2rc_1rc_0$


**SUBTRACT** instruction – **0100**  $ra_3ra_2ra_1ra_0$   $rb_3rb_2rb_1rb_0$   $rc_3rc_2rc_1rc_0$

**HALT** instruction – **0101 0000 0000 0000**


`r's are Register File locations (4 bits each)

`d's are Data Memory locations (8 bits each)

## Refresh – 6-Instruction Processor

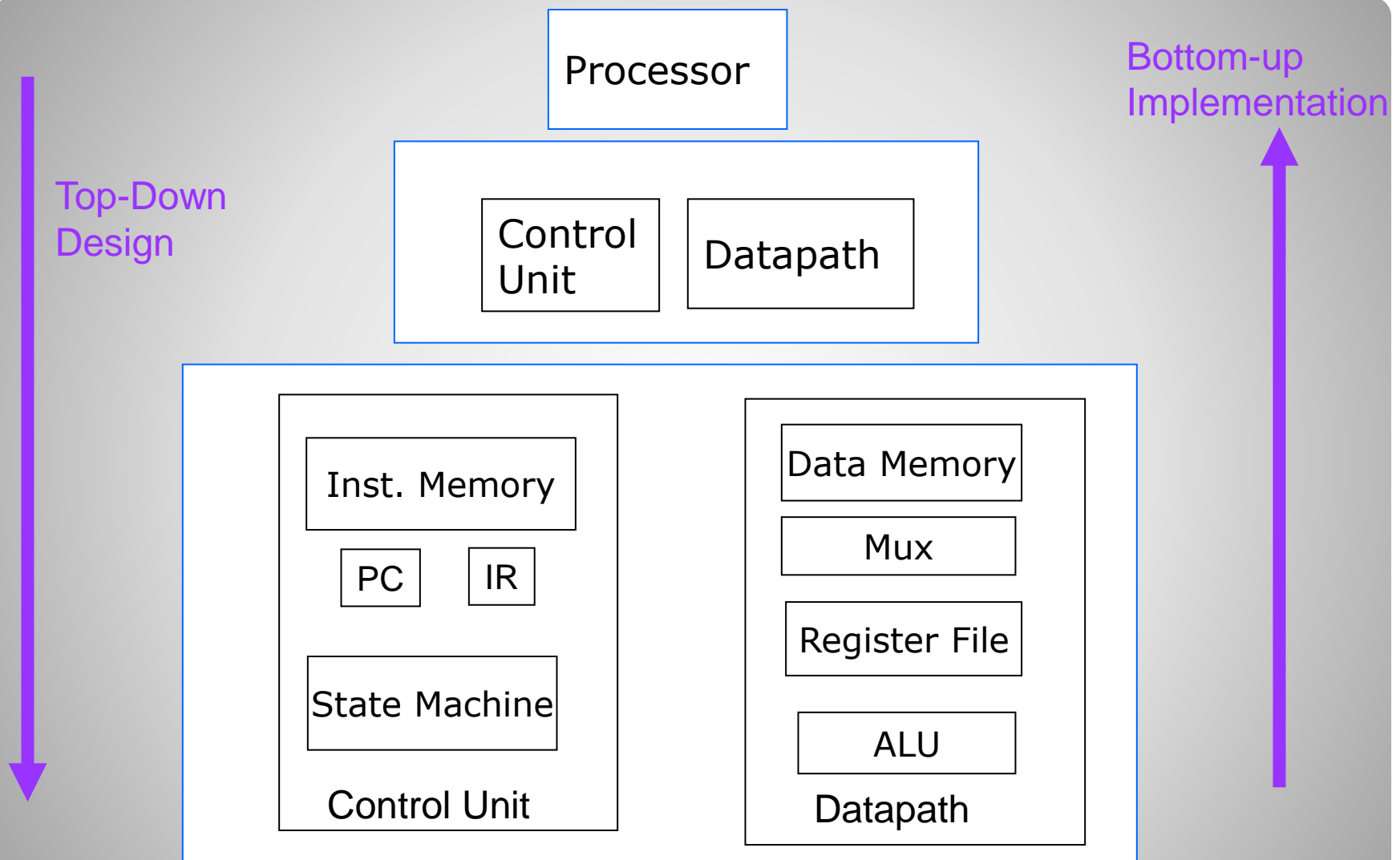


# Pic of Processor Modules

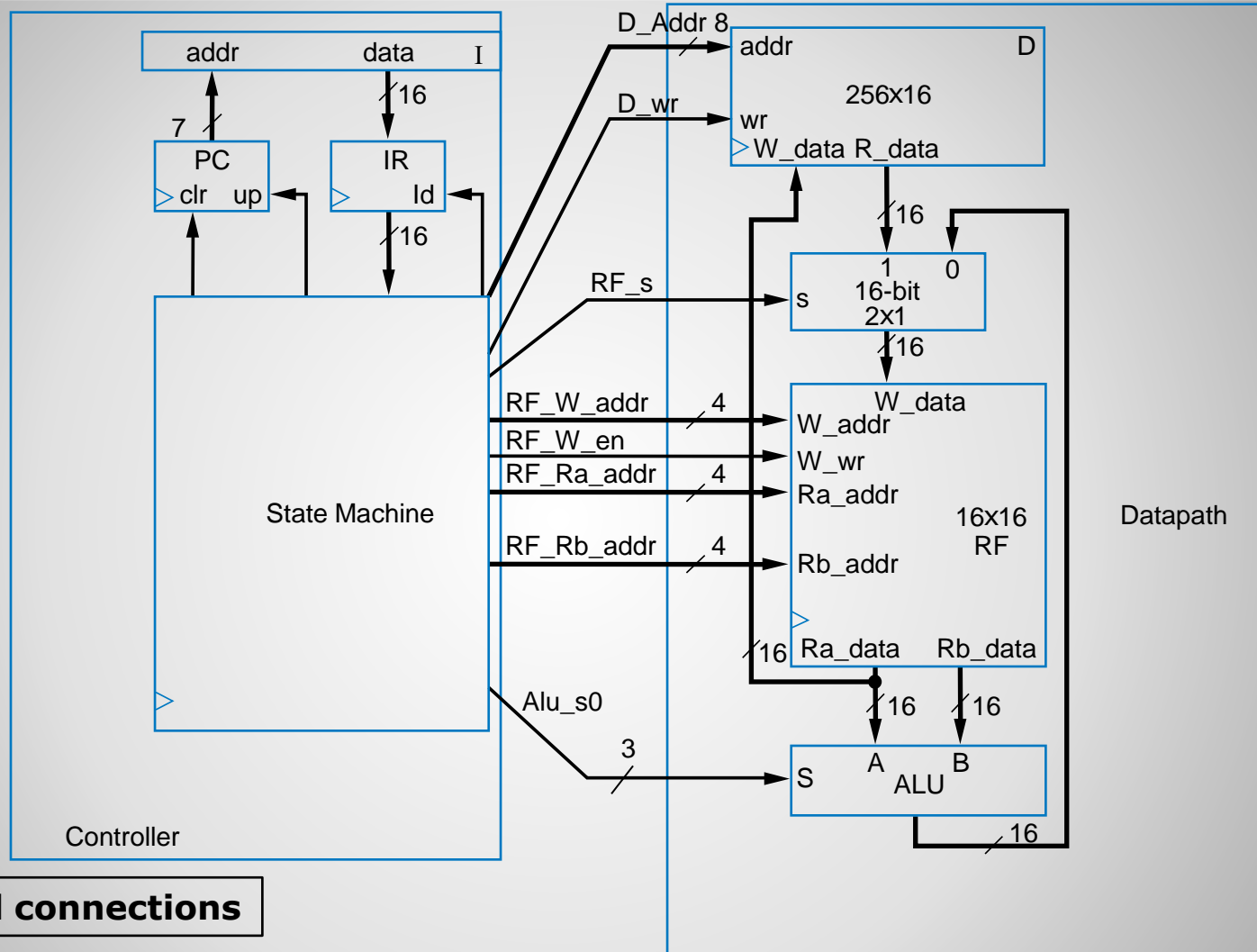

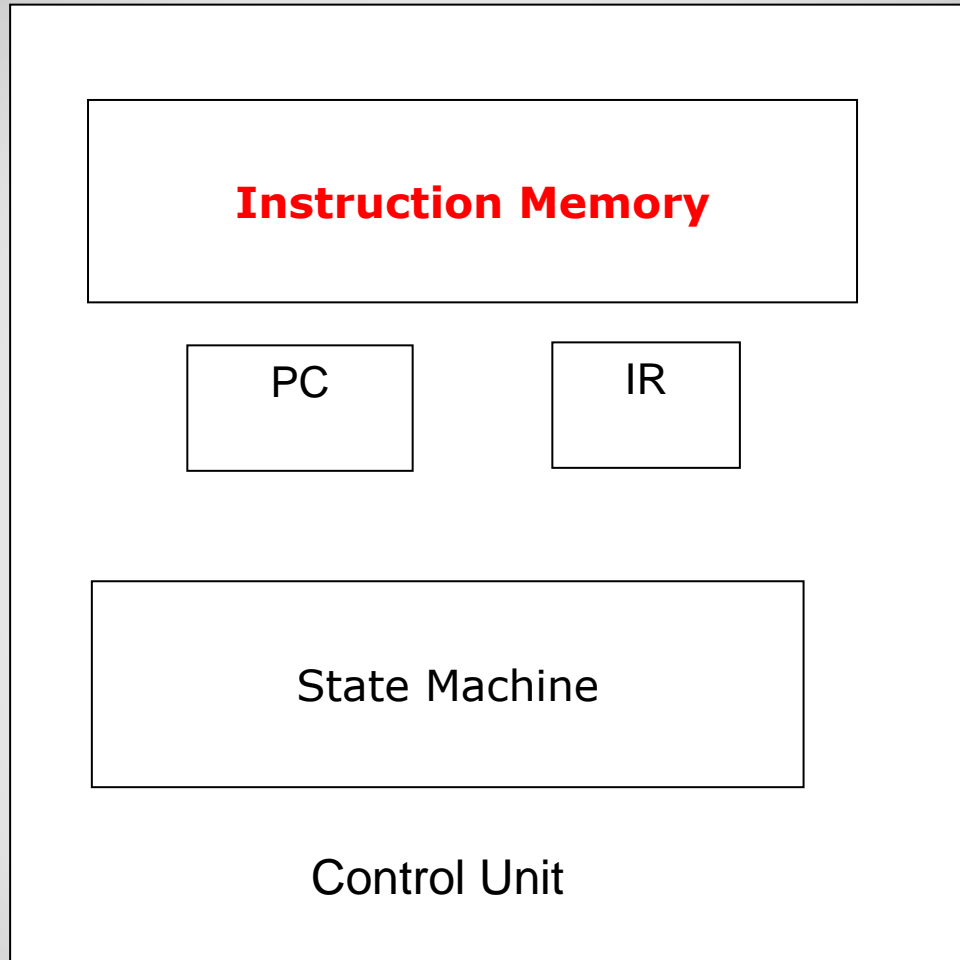**Detailed connections**

**You need to check this pic often  
when connecting multi-modules**



**Along the Control Unit side ...**

- Similar as previous examples
  - Under Quartus, create a new .mif file, name it say, `A.mif`. Later manually type into each location a decimal number converted from your 16-bits instructions.
  - Use Altera Library and build a 1-port ROM module, say, `InstMemory.v`. Make sure during the configuration procedure you have associated `InstMemory.v` with `A.mif`.

## Instruction Memory Module

**How to test the ROM memory?**




Here should be the mif file you created for your RAM/ROM

```
defparam  
    altsyncram_component.clock_enable_input_a = "BYPASS",  
    altsyncram_component.clock_enable_output_a = "BYPASS",  
    altsyncram_component.init_file = "DataMemory.mif",  
    altsyncram_component.intended_device_family = "Cyclone IV E",  
    altsyncram_component.lpm_hint = "ENABLE_RUNTIME_MOD=YES,INSTANCE_NAME=DATA",  
    altsyncram_component.lpm_type = "altsyncram",  
    altsyncram_component.numwords_a = 256,  
    altsyncram_component.operation_mode = "SINGLE_PORT",  
    altsyncram_component.outdata_reg_a = "UNREGISTERED",  
    altsyncram_component.power_up_uninitialized = "FALSE",  
    altsyncram_component.read_during_write_mode_port_a = "NEW_DATA_NO_NBE_READ",  
    altsyncram_component.widthad_a = 8,  
    altsyncram_component.width_a = 16,  
    altsyncram_component.width_byteena_a = 1;
```

Here if showing "clock" change it to be "UNREGISTERED"


# Regarding the memory.v file

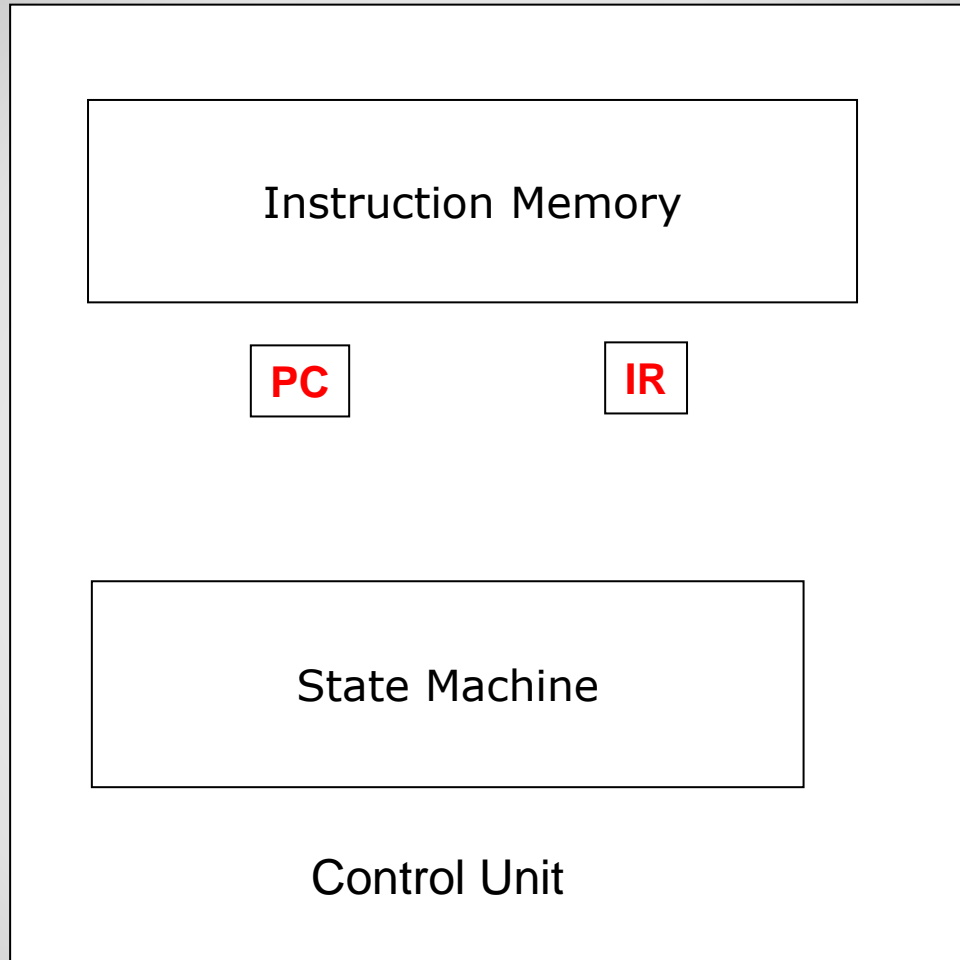


**Along the Control Unit side ...**

- PC is purely a counter
  - Required input signals: Clock, **Clr**, Up
  - Required output signal: address (7-bit) to access instruction memory
  - Notice here **Clr** is active high – from FSM
- IR is purely a group of flip-flops which will latch out the input signal
  - Required input signals: Clock, Id, instruction from instruction memory
  - Required output signal: instruction to the finite state machine



## PC and IR Modules

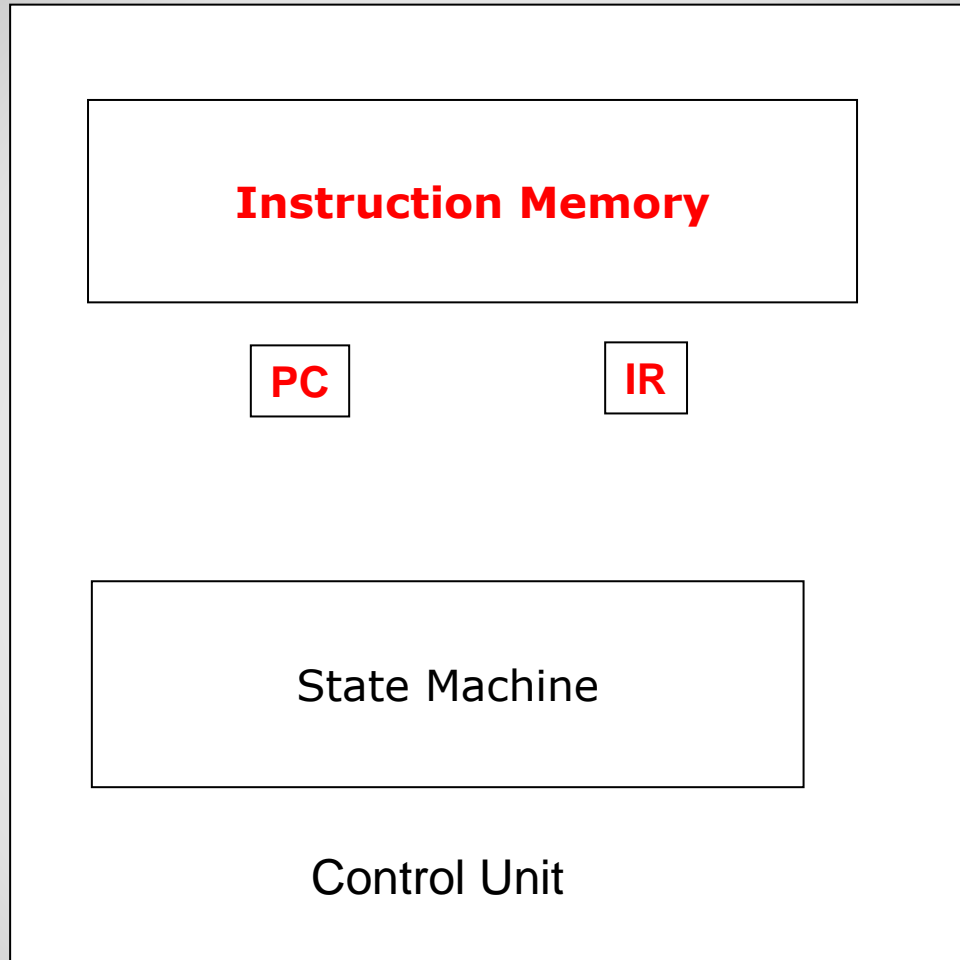

**Combining PC+ROM+IR & Test!**

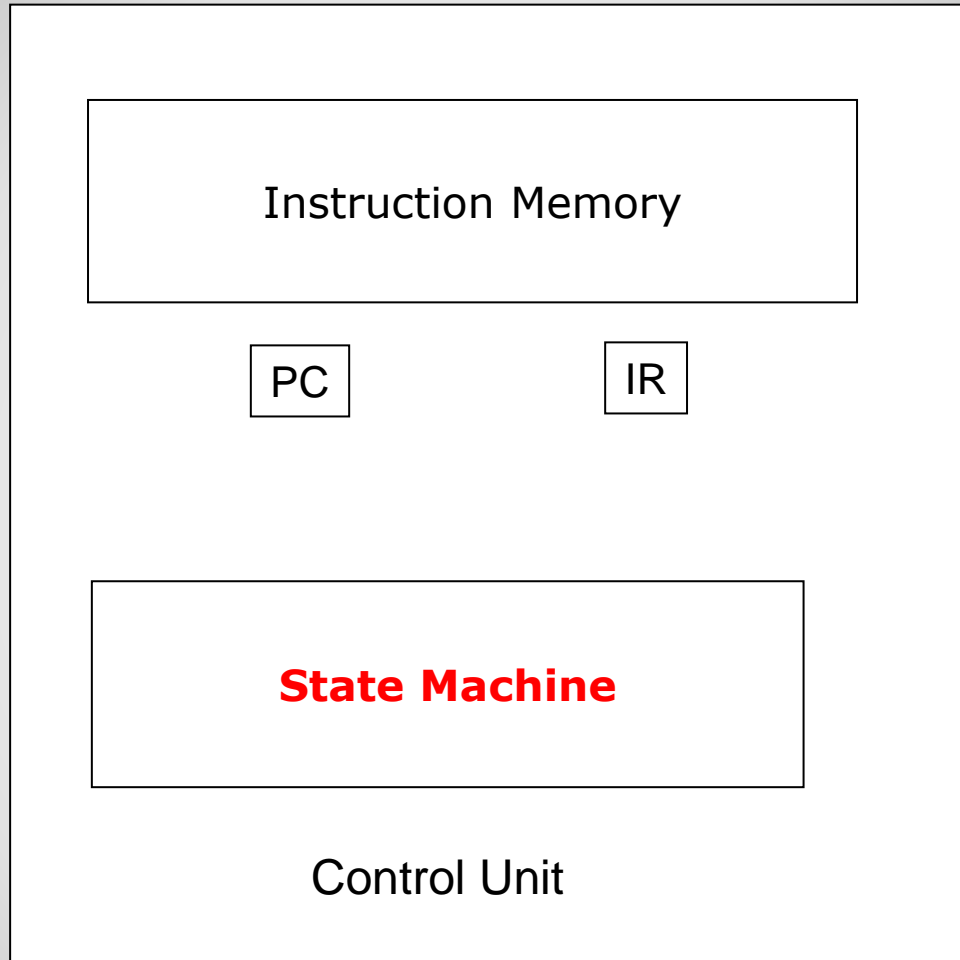


**Along the Control Unit side ...**

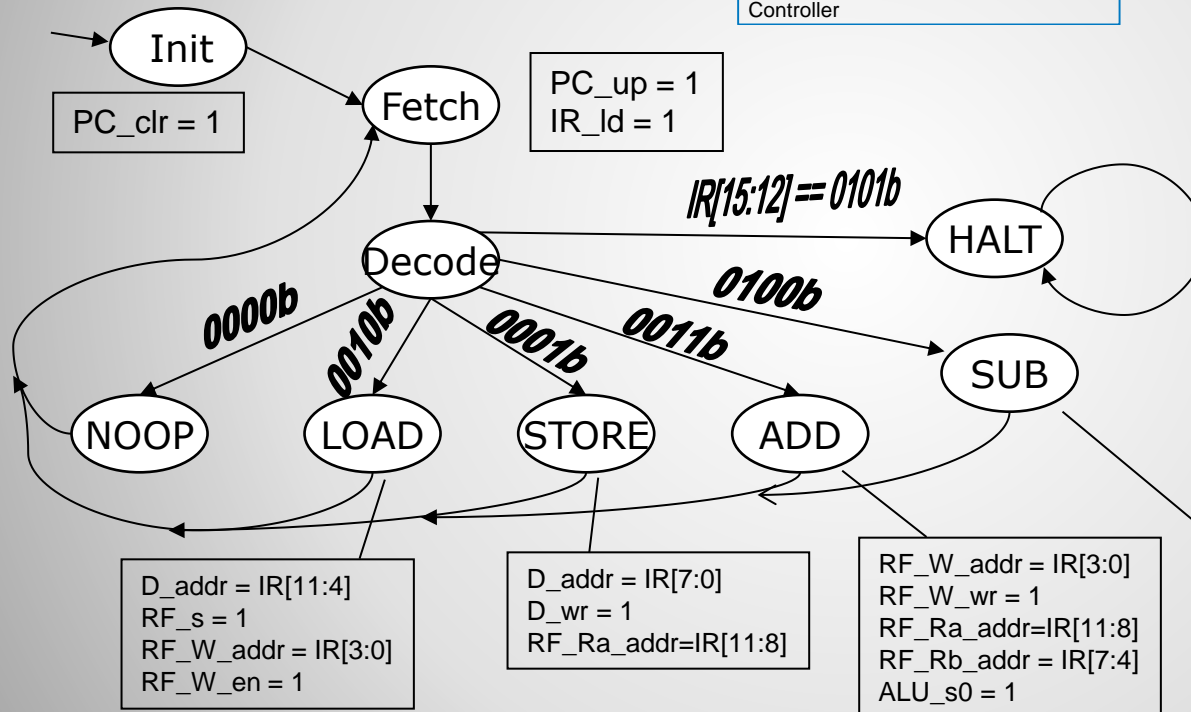 

## Control Lines

Control	Size
PC_clr	1
PC_up	1
IR_Id	1
D_addr	8
D_wr	1
RF_s	1
RF_W_addr	4
RF_W_en	1
RF_Ra_addr	4
RF_Rb_addr	4
Alu_s0	3

# Original State Machine

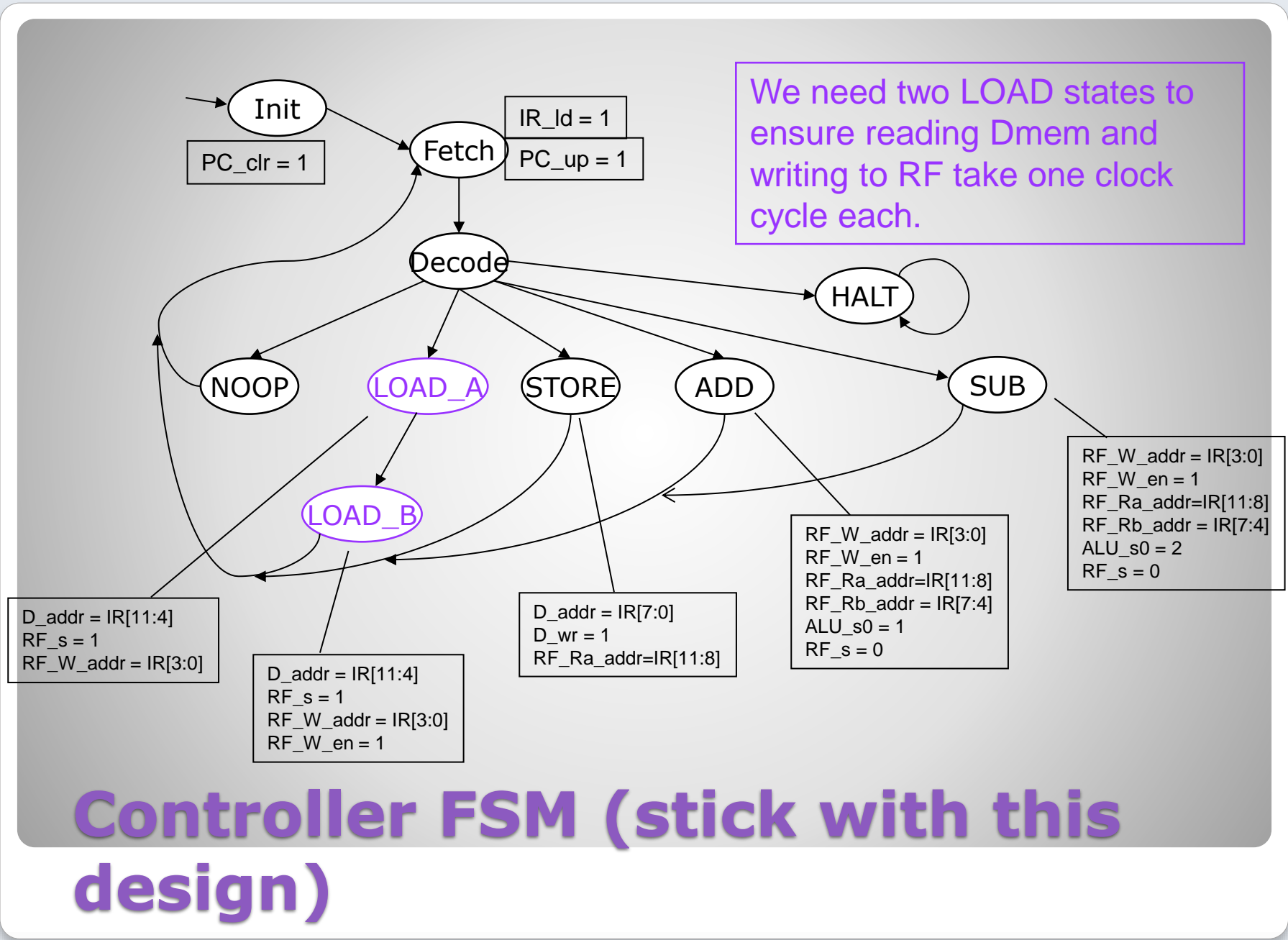

# State Machine Output Definitions


Variable	Meaning
PC_clr	Program counter (PC) clear command
IR_ld	Instruction load command
PC_up	PC increment command
D_addr	Data memory address (8 bits)
D_wr	Data memory write enable
RF_s	Mux select line
RF_Ra_addr	Register file A-side read address (4 bits)
RF_Rb_addr	Register file B-side read address (4 bits)
RF_W_en	Register file write enable
RF_W_Addr	Register file write address (4 bits)
ALU_s0	ALU function select (3 bits)



# State Machine State Outputs

State	Non-Zero Outputs
Init	PC_clr = 1
Fetch	IR_ld = 1, PC_up = 1
Decode	Check the opcode
LoadA	D_addr = IR[11:4], RF_s = 1, RF_W_addr = IR[3:0]
LoadB	D_addr = IR[11:4], RF_s = 1, RF_W_addr = IR[3:0], RF_W_en = 1
Store	D_addr = IR[7:0], D_wr = 1, RF_Ra_addr = IR[11:8]
Add, Sub	RF_Ra_addr = IR[11:8], RF_Rb_addr = IR[7:4], RF_W_addr = IR[3:0], RF_W_en = 1, ALU_s0 = alu function (1 for Add or 2 for Sub), RF_s = 0
Halt	

**How to test the State Machine?**

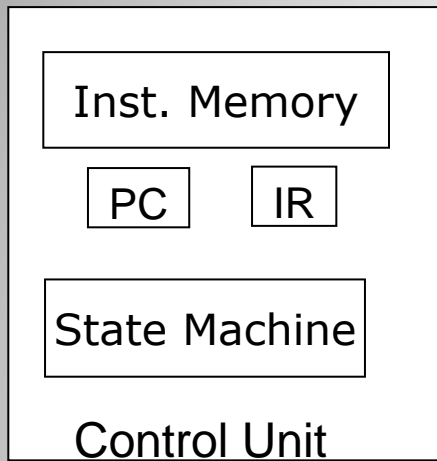

Control Unit module should instantiate the following submodules:

```
PC.sv  
IR.sv  
InstMemory.v  
FSM.sv
```

Required input signals: Clock, ResetN  
(Notice here the ResetN signal is required for FSM; it is active low!)

Required output signals: PC\_Out, IR\_Out, OutState, NextState, D\_Addr, D\_Wr, RF\_s, RF\_W\_en, RF\_Ra\_Addr, RF\_Rb\_Addr, RF\_W\_Addr, ALU\_s0

# Build Control Unit Module and Test it!