

# Programmable Processors

Test Processor  
The Key Conditioner  
Two Clocks .sdc file

- Instruction memory (ROM): 128 X 16
- Data memory (RAM): 256 X 16
- Register file: 16 X 16
- ALU: Two 16-bit inputs, 16-bit output

**Refresh – The Sizes of Things**

- Instruction Set – List of allowable instructions and their representation in memory
- Each of our instructions is **16 bits** long
- Most of them contain some address information
- General form : **operation source destination**

**NOOP** instruction – **0000 0000 0000 0000**

**STORE** instruction – **0001**  $r_3r_2r_1r_0$   $d_7d_6d_5d_4d_3d_2d_1d_0$

**LOAD** instruction – **0010**  $d_7d_6d_5d_4d_3d_2d_1d_0$   $r_3r_2r_1r_0$

**ADD** instruction – **0011**  $ra_3ra_2ra_1ra_0$   $rb_3rb_2rb_1rb_0$   $rc_3rc_2rc_1rc_0$


**SUBTRACT** instruction – **0100**  $ra_3ra_2ra_1ra_0$   $rb_3rb_2rb_1rb_0$   $rc_3rc_2rc_1rc_0$

**HALT** instruction – **0101 0000 0000 0000**


`r's are Register File locations (4 bits each)

`d's are Data Memory locations (8 bits each)

## Refresh – 6-Instruction Processor

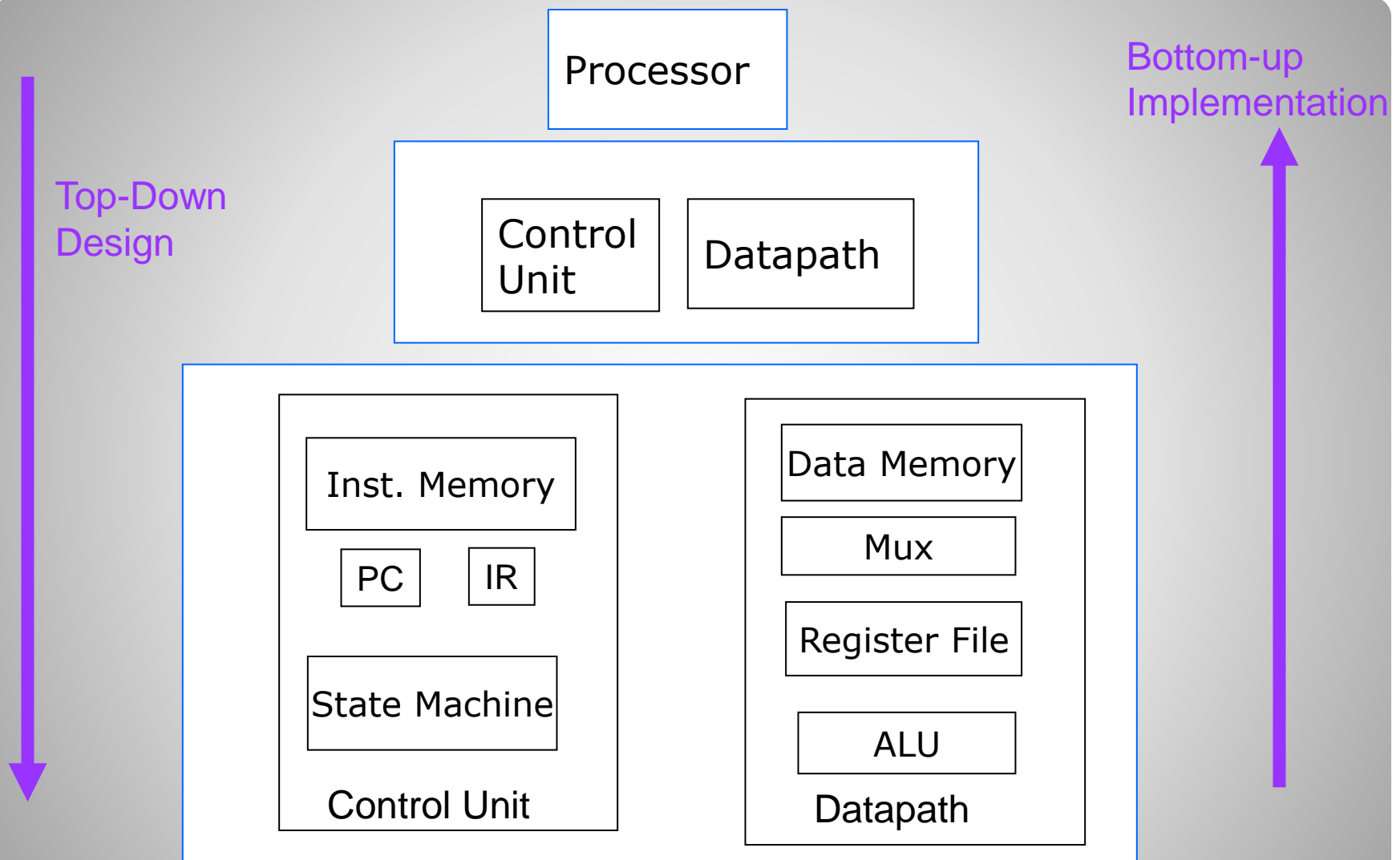

# Pic of Processor Modules

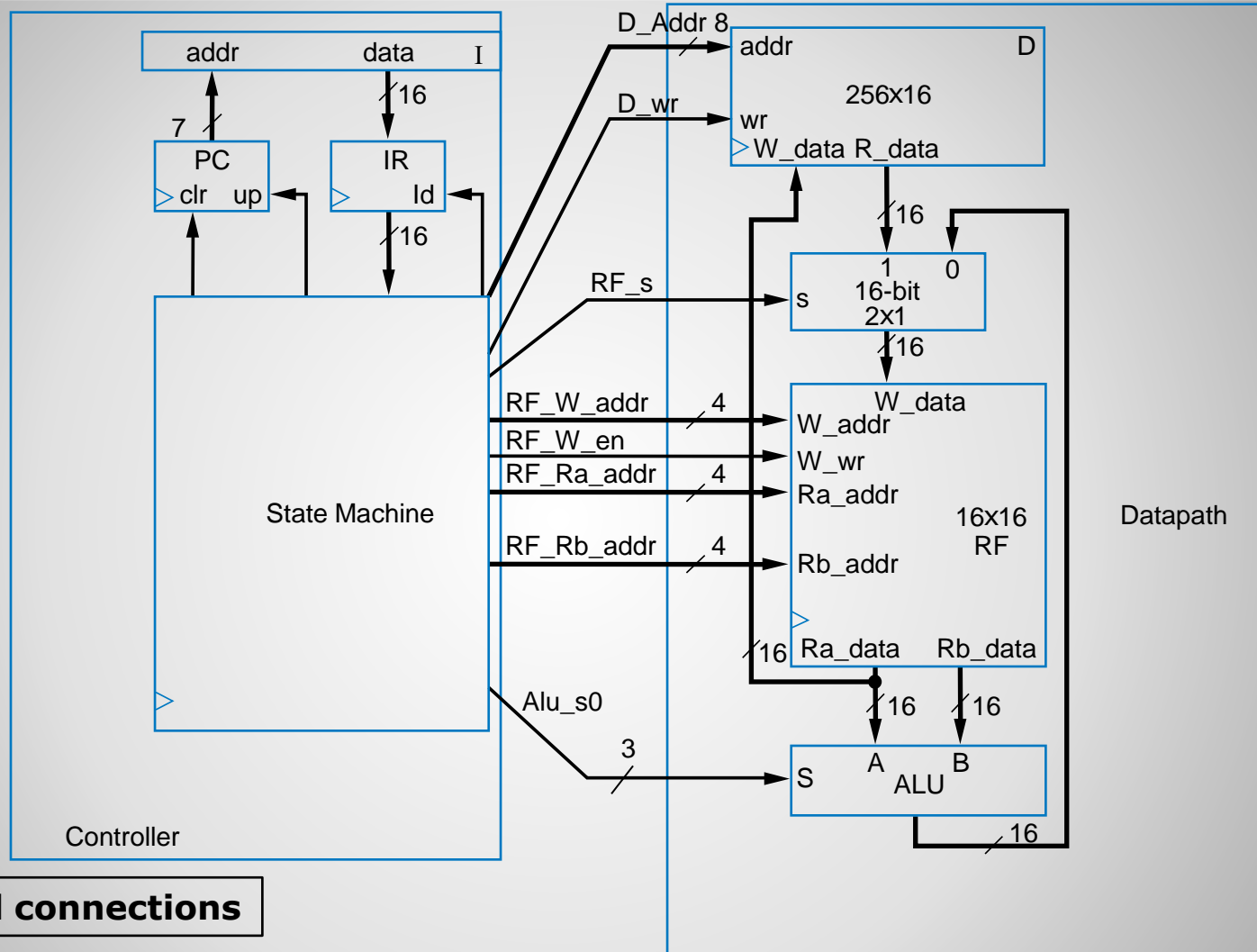

**Detailed connections**

**You need to check this pic often  
when connecting multi-modules**

Processor

Control  
Unit

Datapath

Processor module should instantiate the following submodules:

`ControlUnit.sv`

`DataPath.sv`

Required input signals: Clk, Reset

Required output signals: IR\_Out,  
PC\_Out, State, NextState, ALU\_A,  
ALU\_B, ALU\_Out

**Combine Control Unit and DP in  
Processor Module and Test it!**

- Test submodules from lowest level.
- Test your control unit module and ensure it works as expected
  - Initialize the ROM with translated instructions from Lab4
- Test your datapath module and ensure it works as expected
  - Initialize the RAM with given data in [the project assignment](#)
- Write the Processor by instantiating Control Unit module and Datapath module and wiring them together.
- Test the processor module by running runrtlFSM.do
- At this point you should be able to notice the state machine works but ALU\_A, ALU\_B, and ALU\_out are all zeros.
- Check your memory.v file; revise it as shown on next page
- NOTE: if testing with ModelSim doesn't work it won't help by trying testing on DE2 board.

## Testing your Processor

Here should be the mif file you created for your RAM

```
defparam  
    altsyncram_component.clock_enable_input_a = "BYPASS",  
    altsyncram_component.clock_enable_output_a = "BYPASS",  
    altsyncram_component.init_file = "DataMemory.mif",  
    altsyncram_component.intended_device_family = "Cyclone IV E",  
    altsyncram_component.lpm_hint = "ENABLE_RUNTIME_MOD=YES,INSTANCE_NAME=DATA",  
    altsyncram_component.lpm_type = "altsyncram",  
    altsyncram_component.numwords_a = 256,  
    altsyncram_component.operation_mode = "SINGLE_PORT",  
    altsyncram_component.outdata_aclr_a = "NONE",  
    altsyncram_component.outdata_reg_a = "UNREGISTERED",  
    altsyncram_component.power_up_uninitialized = "FALSE",  
    altsyncram_component.read_during_write_mode_port_a = "NEW_DATA_NO_NBE_READ",  
    altsyncram_component.widthad_a = 8,  
    altsyncram_component.width_a = 16,  
    altsyncram_component.width_byteena_a = 1;
```


Here if showing "clock" change it to be "UNREGISTERED"

# Inside the memory.v file




# The Key Conditioner

Using ButtonSync and a Filter

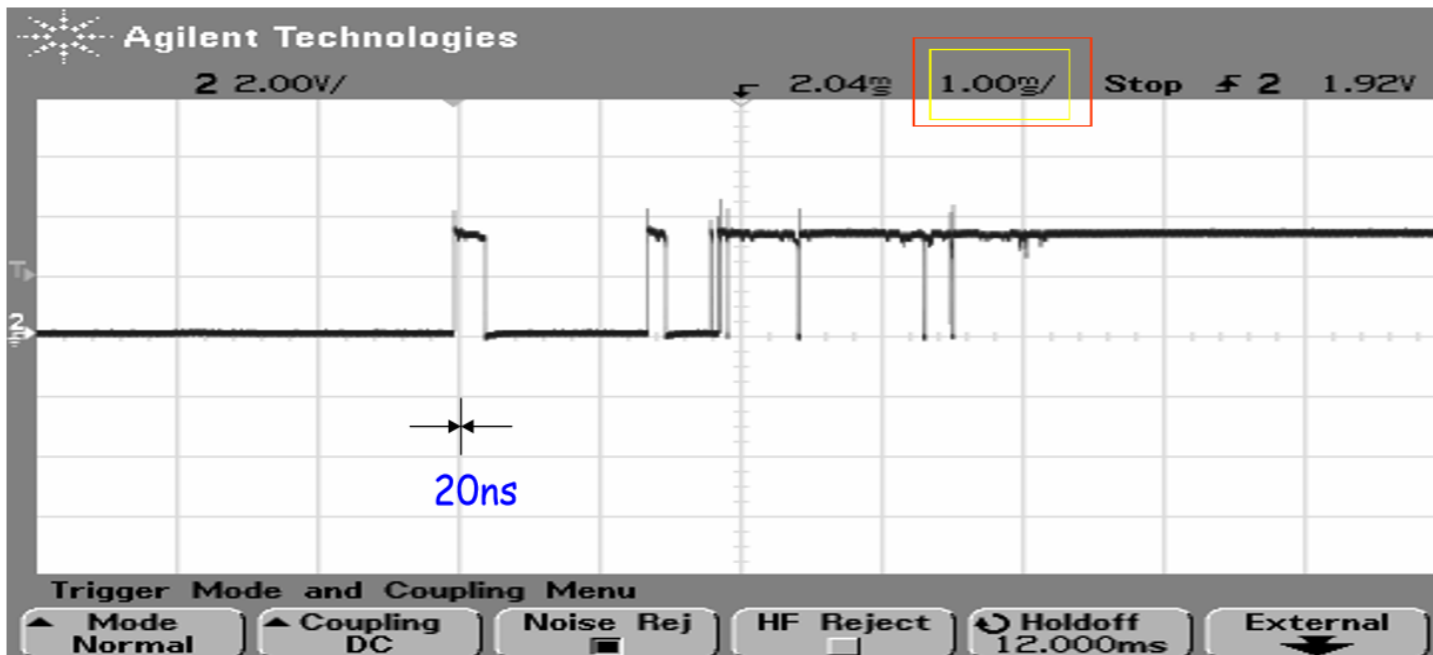

# Mechanical Switch

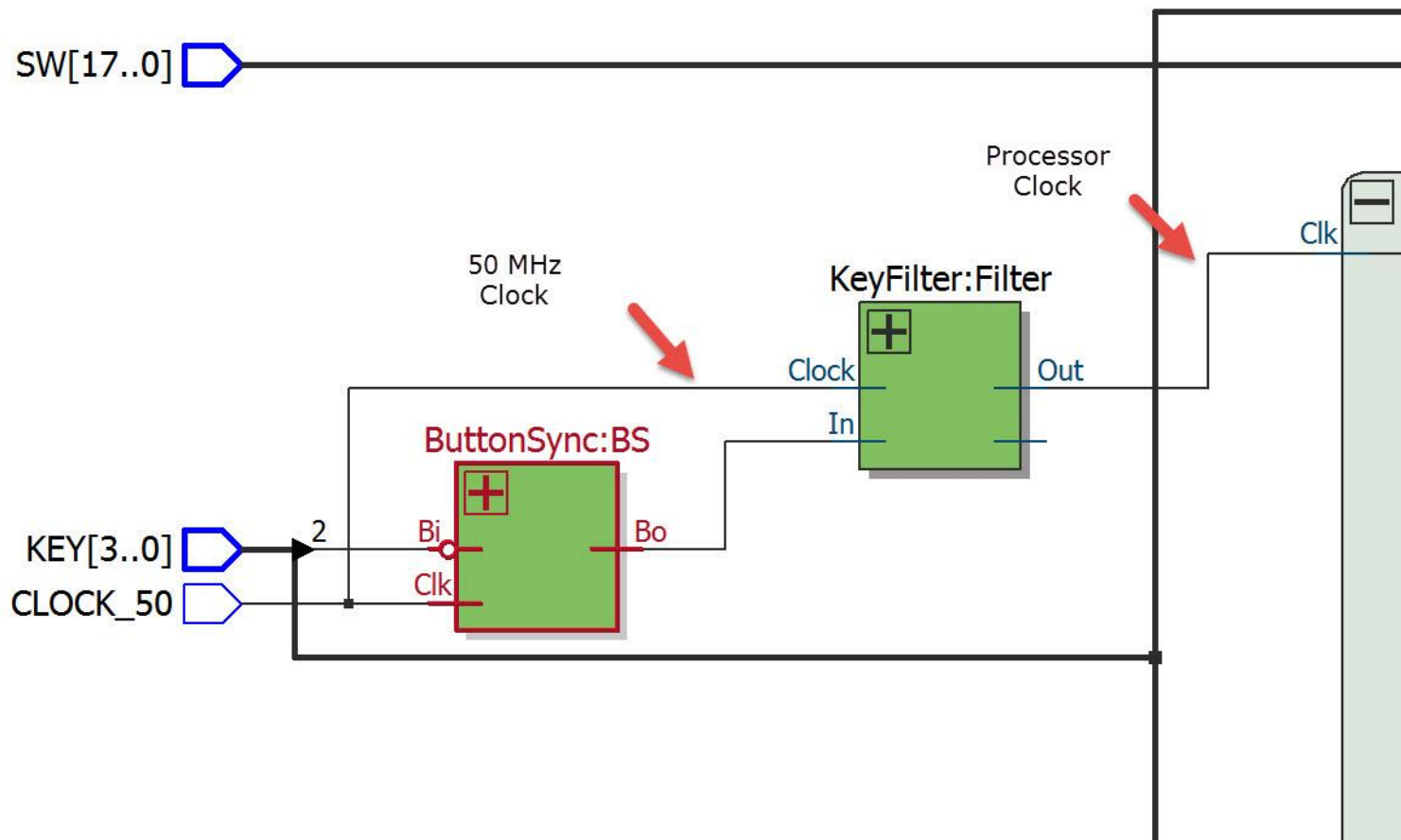

# Key Conditioner

```

//TCES 330 Spring 2025
//The Key Filter follows a button synchronizer
//allows at most 10 output signals per second
//with a 50MHz clock

module KeyFilter (Clk, In, Out);
    input Clk, In;          //Clock and input signal of the system
    output logic Out;       //Output of the filter

    localparam DUR = 5_000_000 - 1;
    logic [32:0] Countdown = 0;

    always @(posedge Clk) begin

        Out <= 0; //initial output value
        if(Countdown == 0) begin
            if(In) begin
                Out <= 1;
                Countdown <= DUR;
            end
        end
        else begin
            Countdown <= Countdown - 1;
        end

    end
endmodule


```

Allows at most 10 output signals per second (assuming a 50 MHz clock).


# Key Filter
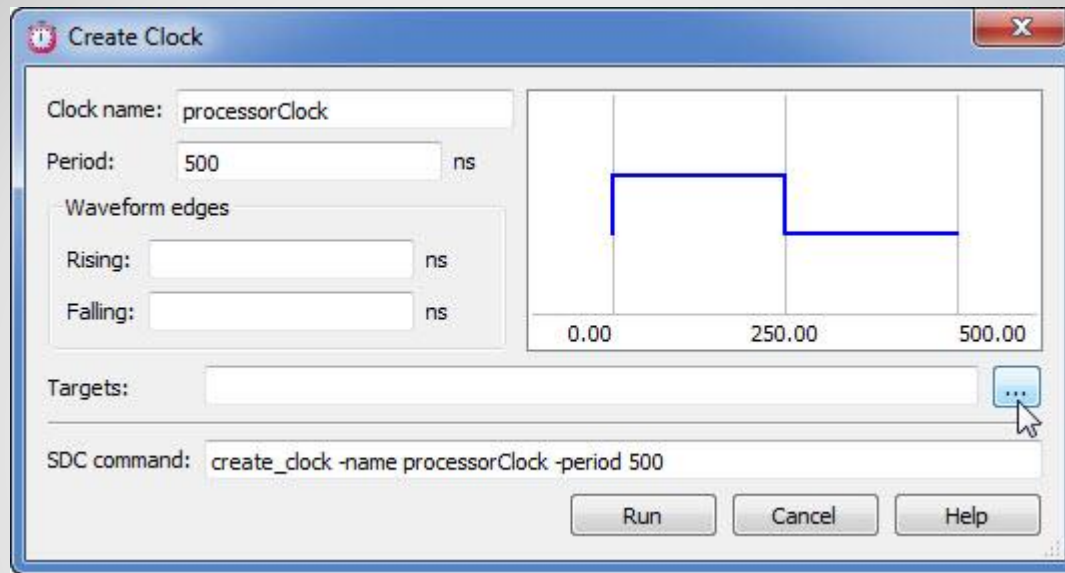
# TimeQuest: Two Clocks


Processor clock (from the KEY) and the 50 MHz clock for the filter circuit



# To Create Processor Clock

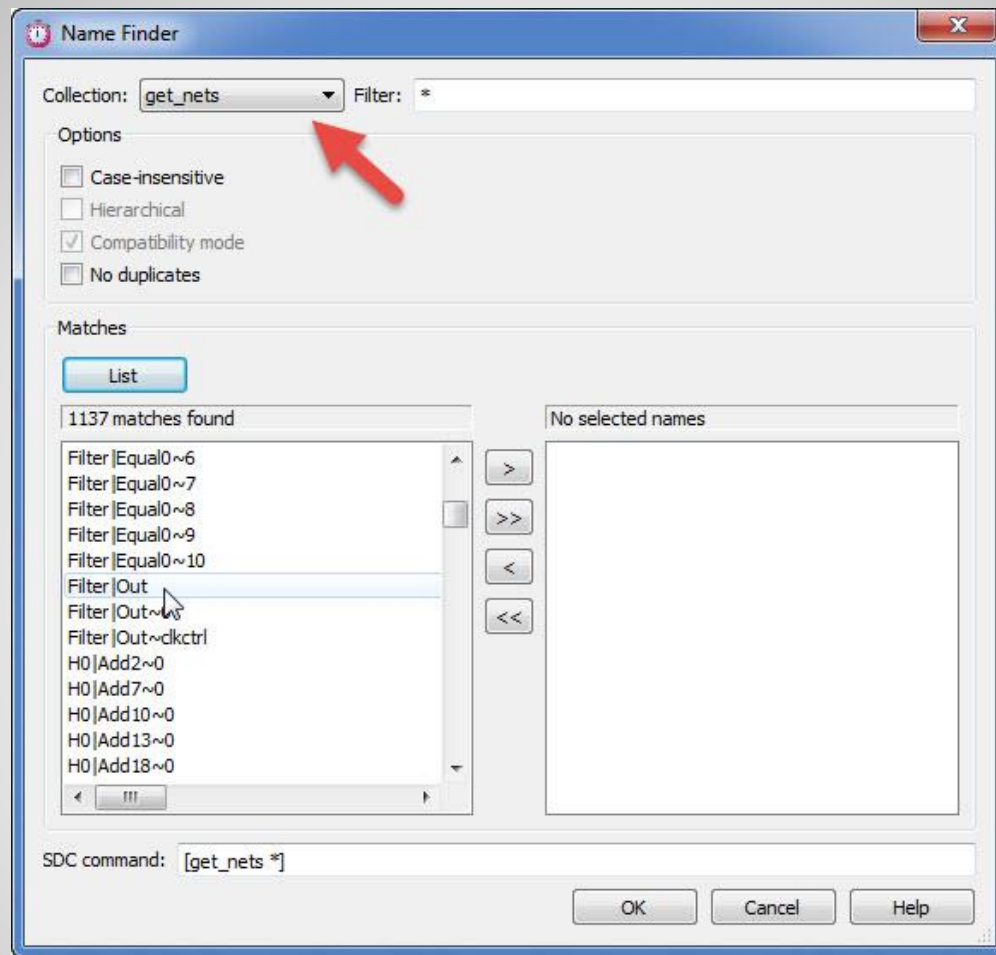


# To Find the Processor Clock

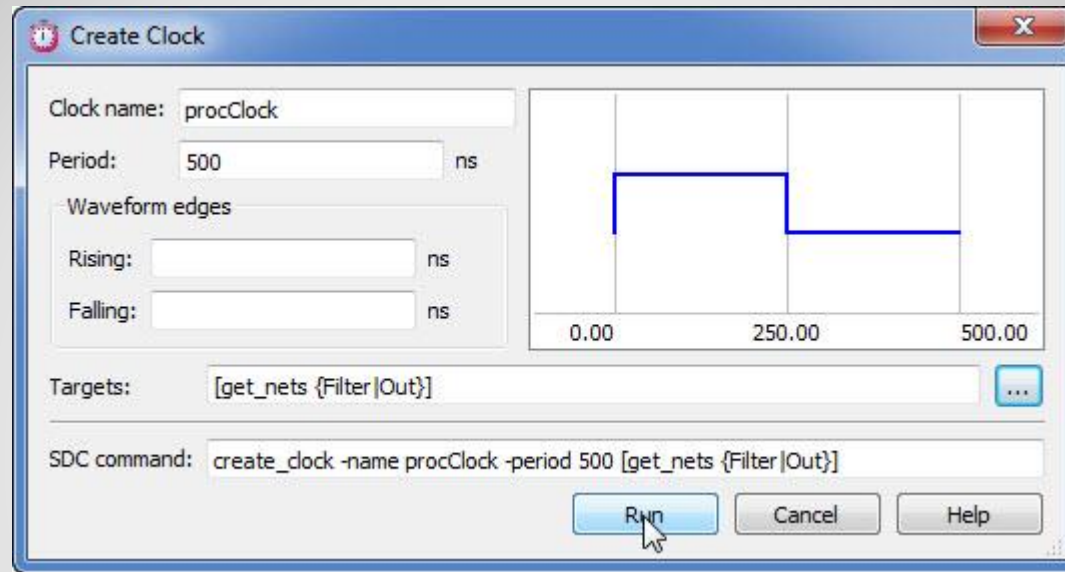

# Run to Create Processor Clock



 

**Create 50 MHz Clock as Usual**

```

36
37
38 #*****
39 # Create Clock
40 #*****
41
42 create_clock -name {sysClock} -period 20.000 -waveform { 0.000 10.000 } [get_ports {CLOCK_50}]
43 create_clock -name {buttonClock} -period 500.000 -waveform { 0.000 250.000 } [get_nets {Filter|Out}]
44
45
46 #*****
47 # Create Generated Clock
48 #*****
49

```

# Your sdc File Should Show Two Clocks

```

#####
# Create Clock
#####

create_clock -name {sysClock} -period 20.000 -waveform { 0.000 10.000 } [get_ports {CLOCK_50}]
create_clock -name {buttonClock} -period 500.000 -waveform { 0.000 250.000 } [get_nets {KF|Out}]
create_clock -name {altera_reserved_tck} -period 100.000 -waveform { 0.000 50.000 } [get_ports {altera_reserved_tck}]

#####
# Create Generated Clock
#####

#####
# Set Clock Latency
#####

#####
# Set Clock Uncertainty
#####

set_clock_uncertainty -rise_from [get_clocks {buttonClock}] -rise_to [get_clocks {buttonClock}] 1.000
set_clock_uncertainty -rise_from [get_clocks {buttonClock}] -fall_to [get_clocks {buttonClock}] 1.000
set_clock_uncertainty -fall_from [get_clocks {buttonClock}] -rise_to [get_clocks {buttonClock}] 1.000
set_clock_uncertainty -fall_from [get_clocks {buttonClock}] -fall_to [get_clocks {buttonClock}] 1.000
set_clock_uncertainty -rise_from [get_clocks {sysClock}] -rise_to [get_clocks {sysClock}] 1.000
set_clock_uncertainty -rise_from [get_clocks {sysClock}] -fall_to [get_clocks {sysClock}] 1.000
set_clock_uncertainty -fall_from [get_clocks {sysClock}] -rise_to [get_clocks {sysClock}] 1.000
set_clock_uncertainty -fall_from [get_clocks {sysClock}] -fall_to [get_clocks {sysClock}] 1.000
set_clock_uncertainty -rise_from [get_clocks {altera_reserved_tck}] -fall_to [get_clocks {altera_reserved_tck}] 1.000
set_clock_uncertainty -fall_from [get_clocks {altera_reserved_tck}] -rise_to [get_clocks {altera_reserved_tck}] 1.000
set_clock_uncertainty -rise_from [get_clocks {altera_reserved_tck}] -rise_to [get_clocks {altera_reserved_tck}] 1.000
set_clock_uncertainty -fall_from [get_clocks {altera_reserved_tck}] -fall_to [get_clocks {altera_reserved_tck}] 1.000

```

# In Some Cases, .sdc File Needs to Include a Third Clock