

# Programmable Processors

Datapath operation

- Instruction memory (ROM): 128 X 16
- Data memory (RAM): 256 X 16
- Register file: 16 X 16
- ALU: Two 16-bit inputs, 16-bit output

**Refresh – The Sizes of Things**

- Instruction Set – List of allowable instructions and their representation in memory
- Each of our instructions is **16 bits** long
- Most of them contain some address information
- General form : **operation source destination**

**NOOP** instruction – **0000 0000 0000 0000**

**STORE** instruction – **0001**  $r_3r_2r_1r_0$   $d_7d_6d_5d_4d_3d_2d_1d_0$

**LOAD** instruction – **0010**  $d_7d_6d_5d_4d_3d_2d_1d_0$   $r_3r_2r_1r_0$

**ADD** instruction – **0011**  $ra_3ra_2ra_1ra_0$   $rb_3rb_2rb_1rb_0$   $rc_3rc_2rc_1rc_0$


**SUBTRACT** instruction – **0100**  $ra_3ra_2ra_1ra_0$   $rb_3rb_2rb_1rb_0$   $rc_3rc_2rc_1rc_0$

**HALT** instruction – **0101 0000 0000 0000**


`r's are Register File locations (4 bits each)

`d's are Data Memory locations (8 bits each)

## Refresh – 6-Instruction Processor

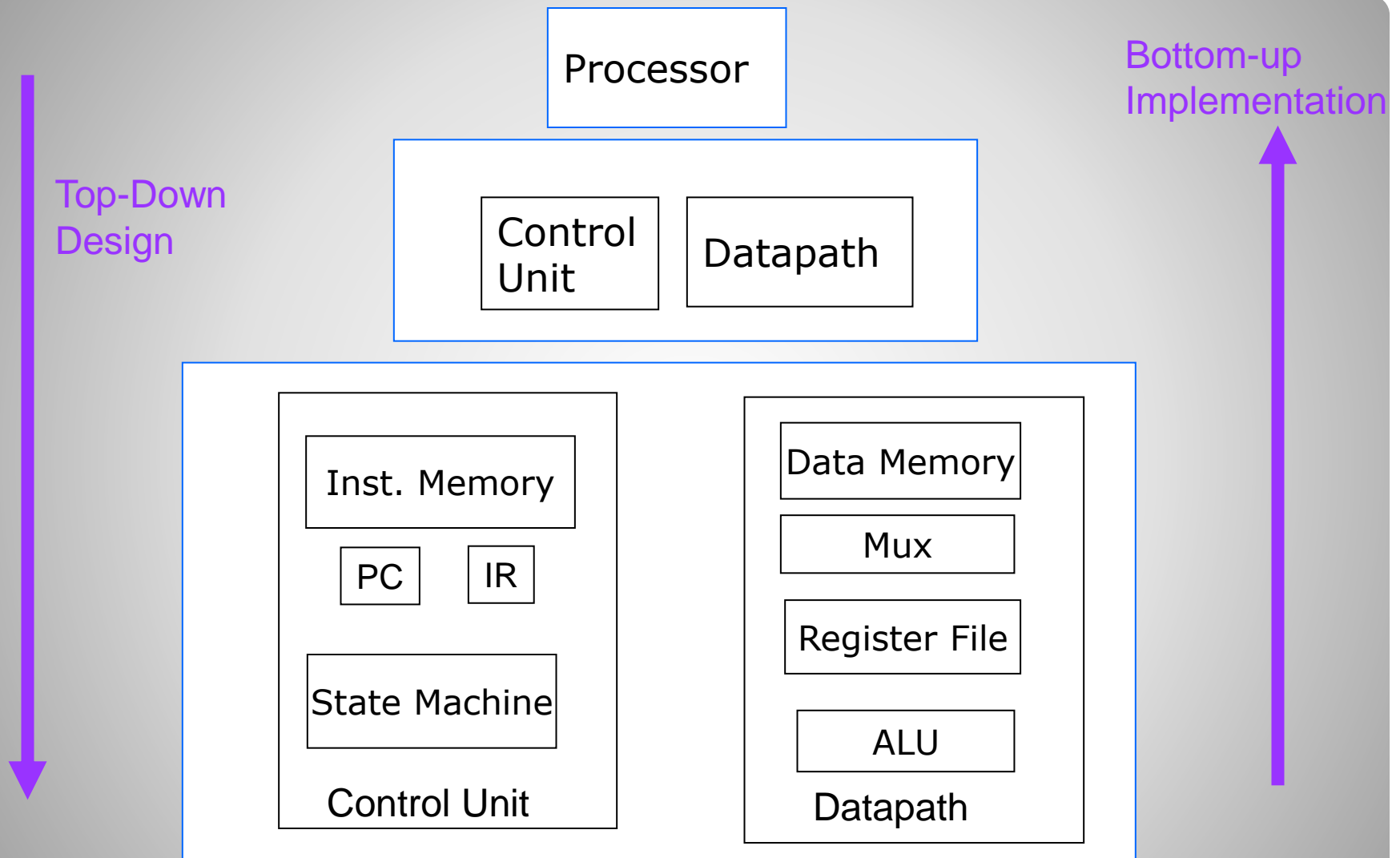


# Pic of Processor Modules

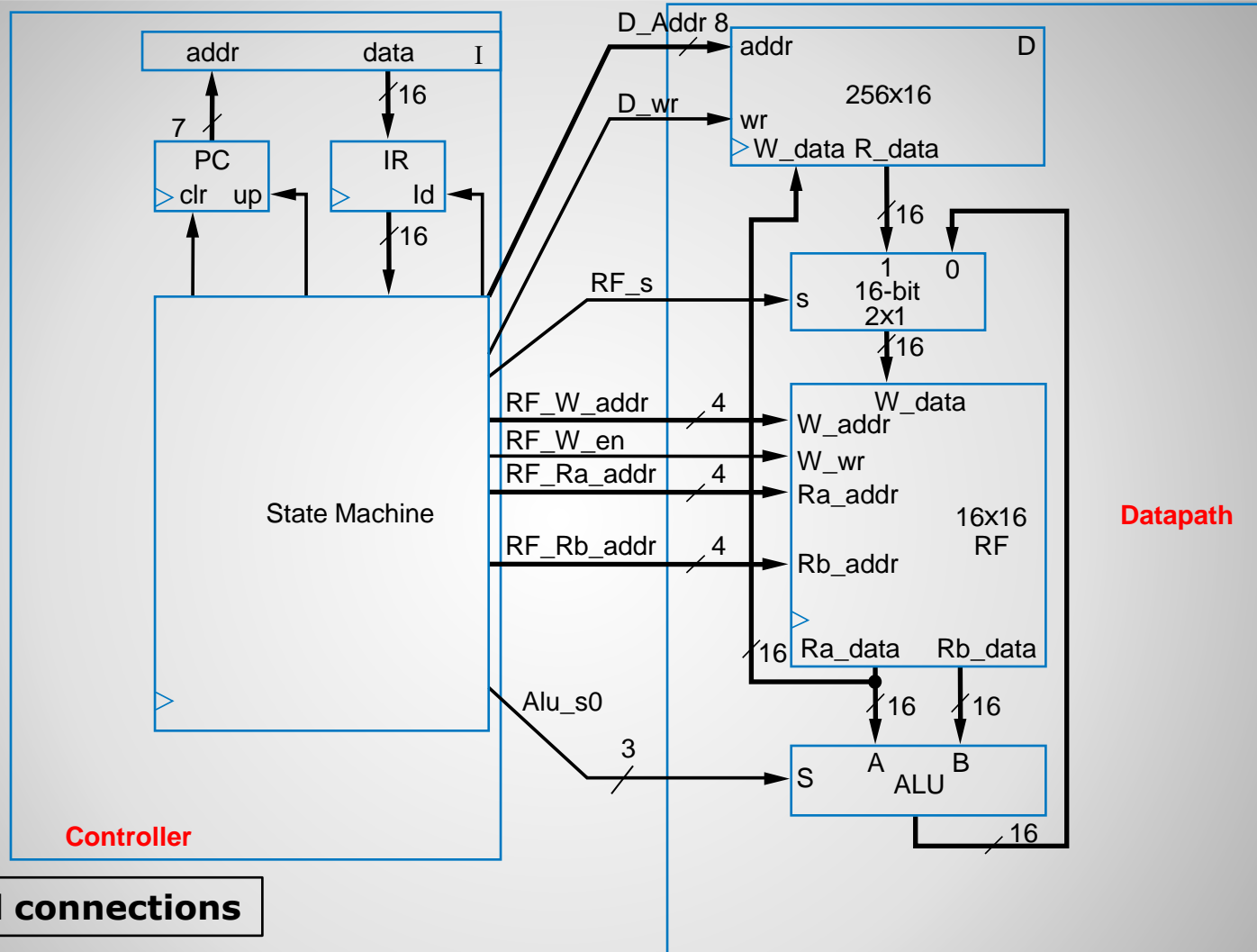


**Detailed connections**

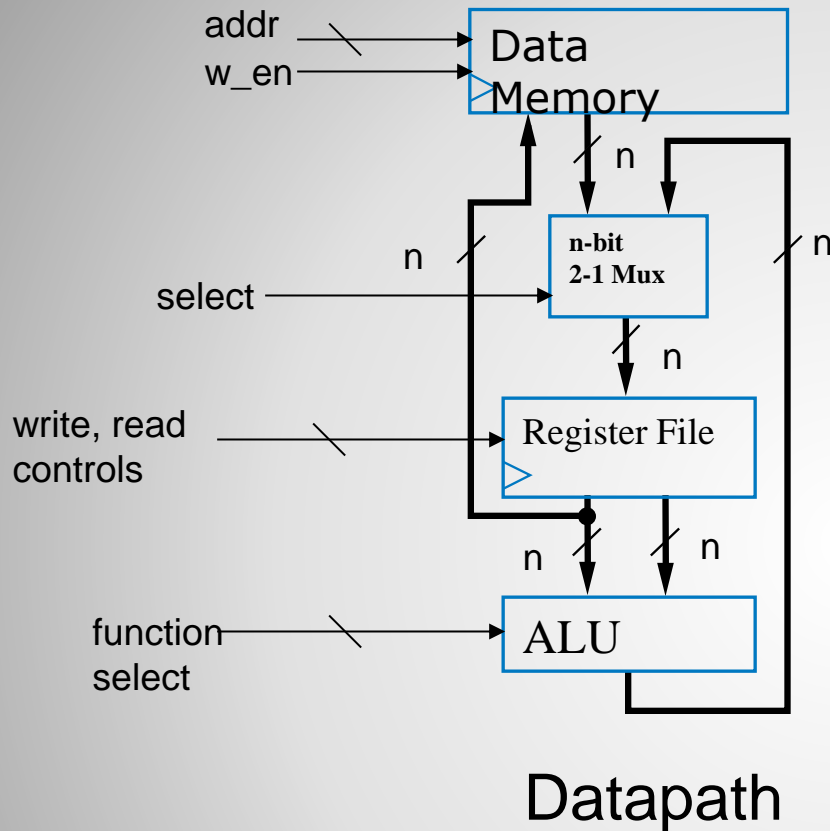**You need to check this pic often when connecting multi-modules**




- Takes data from Data Memory
- Stores it in Register File
- Operates on it in ALU (puts it back into the Register File)
- Can store Register File data back into Data Memory
- Note the dual output Register File


# Datapath Side

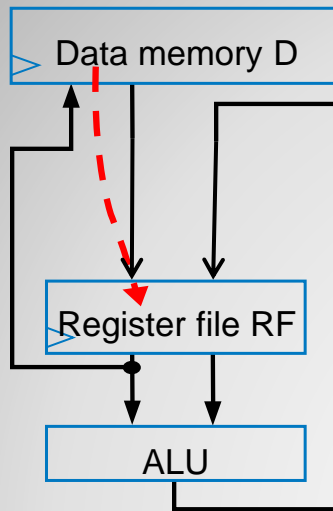

LOAD operation

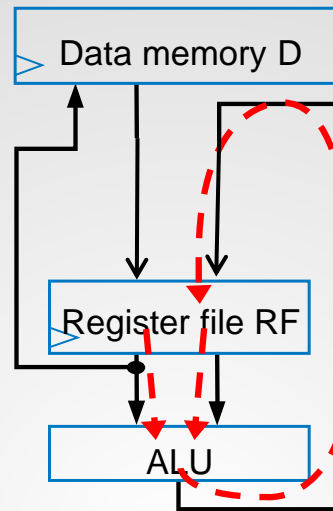

ALU operation  
(like an ADD)

 

STORE operation

$D[9] = D[0] + D[1]$  – requires a sequence of four datapath operations:

LOAD 0:  $RF[0] = D[0]$


LOAD 1:  $RF[1] = D[1]$

ADD 2:  $RF[2] = RF[0] + RF[1]$

STORE3:  $D[9] = RF[2]$

Each line here represents one instruction; so it takes four instructions to do this add

# Basic Datapath Operations

 

# The Register File



```
// This is a Verilog description for an 8 x 16 register file
module regfile8x16a
  (input clk,                // system clock
   input write,              // write enable
   input [2:0] wrAddr,       // write address
   input [15:0] wrData,      // write data
   input [2:0] rdAddrA,      // A-side read address
   output [15:0] rdDataA,    // A-side read data
   input [2:0] rdAddrB,      // B-side read address
   output [15:0] rdDataB ); // B-side read data

  logic [15:0] regfile [0:7]; // 8 registers, each 16-bit

  // read the registers
  ..... // put your code here

  // write the registers
  ..... // put your code here

endmodule
```

# Register File (for reference)

```

module registerfile (Read1,Read2,WriteReg,WriteData,RegWrite,
Data1,Data2,clock);

    input [5:0] Read1,Read2,WriteReg; // the register numbers
    to read or write
    input [31:0] WriteData; // data to write
    input RegWrite, // the write control
    clock; // the clock to trigger write
    output [31:0] Data1, Data2; // the register values read
    reg [31:0] RF [31:0]; // 32 registers each 32 bits long

    assign Data1 = RF[Read1];
    assign Data2 = RF[Read2];

    always begin
        // write the register with new value if Regwrite is
        high
        @(posedge clock) if (RegWrite) RF[WriteReg] <=
        WriteData;
    end

endmodule

```

**read the registers**

**Write to the registers**

**FIGURE B.8.11** A MIPS register file written in behavioral Verilog.  
This register file writes on the rising clock edge.

## A MIPS register file (372 Textbook)

**How to test the register file?**

**Data Memory**

Mux

Register File

ALU

Datapath

**Along the Datapath side**

- Follow instructions:
  - Under Quartus, create a new .mif file, name it say, `D.mif`. Later manually type into specific locations numbers according to the given requirements.
  - Use Altera Library and build a 1-port RAM module, say, `DataMemory.v`. Make sure during the configuration procedure you have associated `DataMemory.v` with `D.mif`.

## Data Memory Module

**How to test the Data Memory?**


**Data Memory**

**Register File**

ALU

Datapath

**Connect Reg and Dmem & Test!**

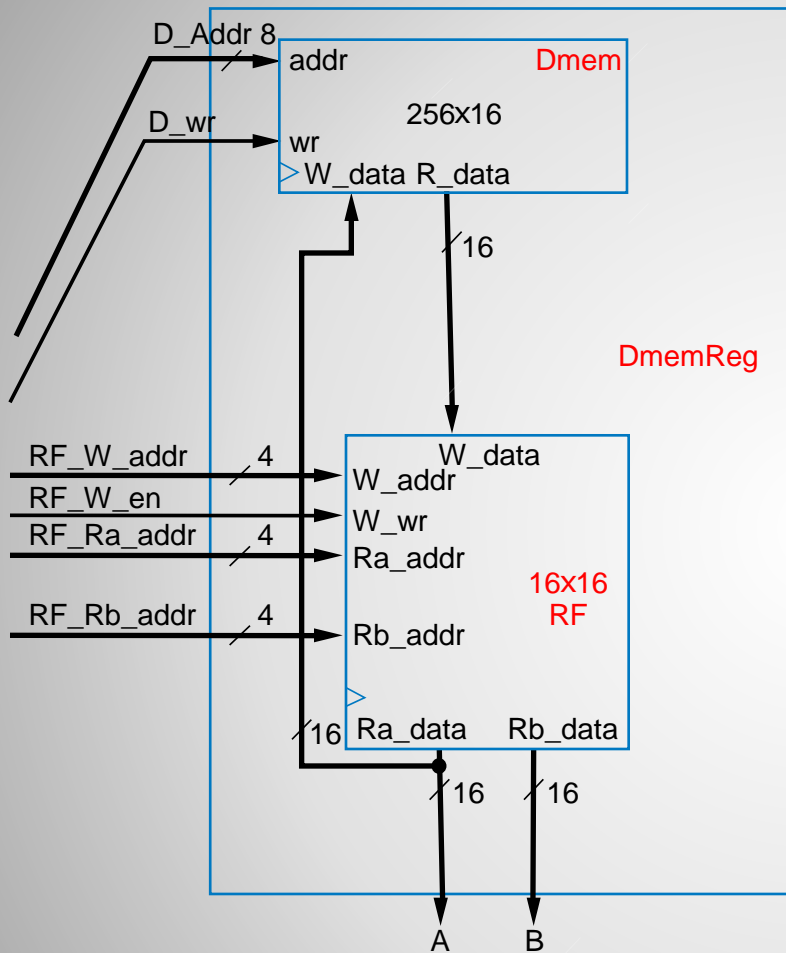

# Design and Test of DmemReg




Data Memory

**Register File**


**ALU**

Datapath

**Connect Reg and ALU & Test!**

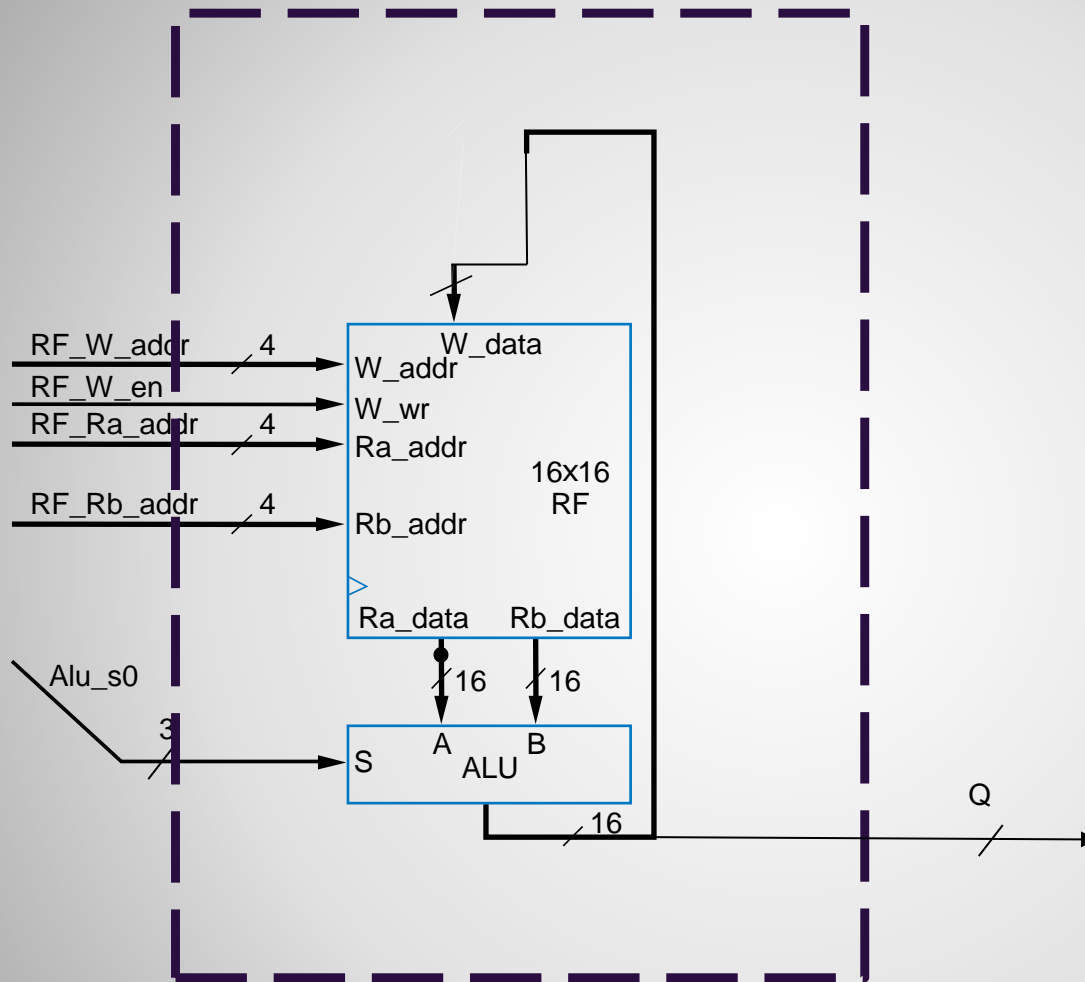

**Connect Reg and ALU & Test!**

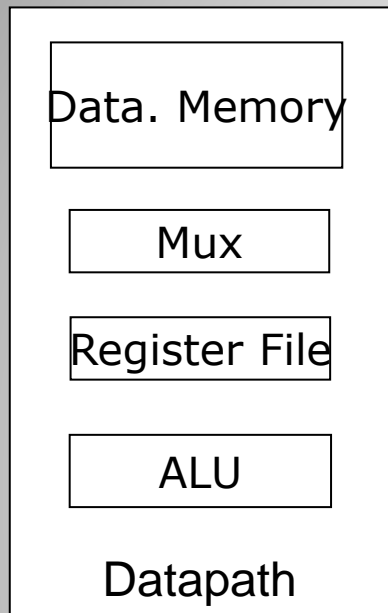

Datapath module should instantiate the following submodules:

```
DataMemory.v  
Mux.sv  
Register.sv  
ALU.sv
```

Required input signals: Clock, D\_Addr, D\_Wr, RF\_s, RF\_W\_Addr, RF\_W\_en, RF\_Ra\_Addr, RF\_Rb\_Addr, ALU\_s0

Required output signals: ALU\_inA, ALU\_inB, ALU\_out

**Connect all 4 modules to build  
Datapath Module & Test!**